

Lab Report – 5bit DAC

Course: VLSI

Date: 09/25/2025

Abstract

This experiment investigates the design and simulation of digital-to-analog converters (DACs) using resistive networks. The work begins with the analysis of a basic resistor voltage divider, which is then extended into a 5-bit ladder DAC. Circuit schematics, layouts, and LTspice simulations were performed to evaluate performance. Results show that the voltage divider divides an input of 1 V into ~ 0.333 V output, and the 5-bit DAC provides correct binary-weighted outputs consistent with theory.

Introduction

A voltage divider is the simplest resistive circuit that scales down an input voltage by a fixed ratio. It forms the foundation of more complex circuits such as the R-2R ladder, which is a widely used architecture for digital-to-analog conversion due to its simplicity and scalability.

In the DAC, only two resistor values (R and $2R$) are required regardless of bit resolution, ensuring uniformity and accuracy. The DAC converts binary digital signals into analog voltages by summing weighted contributions of each bit. Such DACs are used in microcontrollers, signal processing, and communication systems.

Materials and Methods

Software Tools:

- Electric VLSI for schematic/layout design
- LTspice for circuit simulation

Components:

- Resistors: $10\text{ k}\Omega$ (used for both R and $2R$ equivalents)

Procedure:

1. Designed a voltage divider circuit in Electric VLSI.
2. Exported netlist and simulated in LTspice to confirm voltage scaling.
3. Designed a 5-bit DAC using cascaded resistor ladders.
4. Implemented both schematic and layout, including 3D layout verification.
5. Ran DC operating point and transient simulations in LTspice.

Results


Voltage Divider Input

voltage: $V_{in} = 1\text{ V}$


Simulation output:

- Midpoint node: $\sim 0.667\text{ V}$
- V_{out} : $\sim 0.333\text{ V}$
- Current through resistors: $\sim 33\text{ }\mu\text{A}$

Voltage Divider Schematic:

 

Voltage Divider Layout:

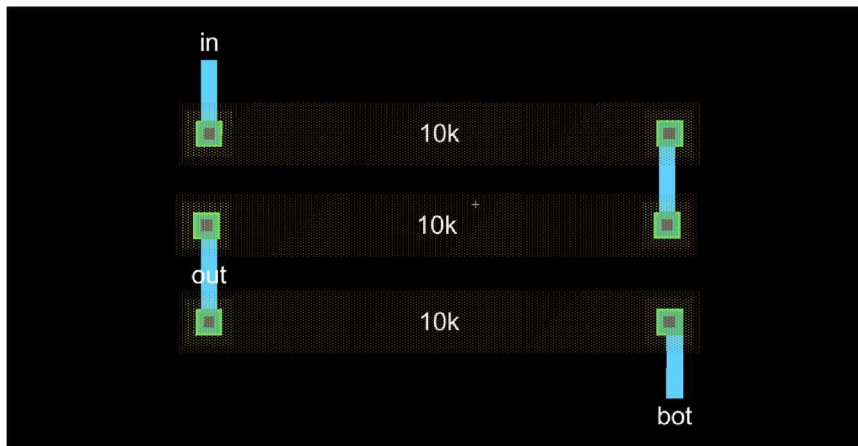

Resistance is determined by the material's sheet resistance R_s (Ω/square):


$$R = R_s \cdot \frac{L}{W}$$

To get exactly R and $2R$, the ratio L/W is adjusted. For example:

$$R = R_s \cdot \frac{L}{W}$$

$$2R = R_s \cdot \frac{2L}{W} \text{ (or same length, half width).}$$


LTspice Simulation Result:

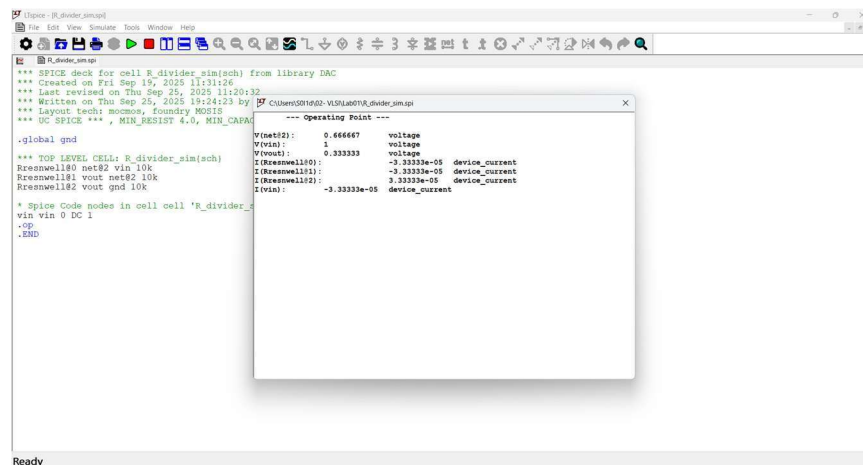

5-bit DAC

Binary inputs (b4...b0) connected to reference voltages.

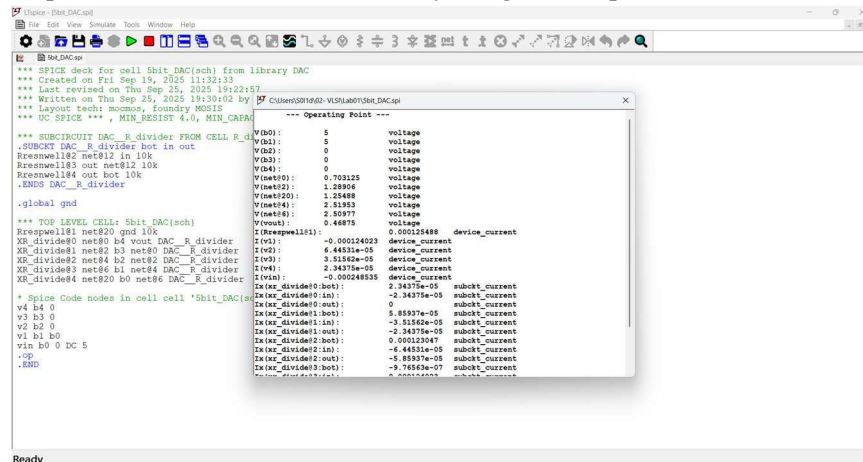LTspice simulations confirmed binary-weighted outputs.




Sample LTspice results (Operating Point):

- b4=1, b3=0, b2=0, b1=0, b0=0 → Vout ≈ 0.703 V
- b4=1, b3=1, b2=0, b1=0, b0=0 → Vout ≈ 1.289 V
- b4=1, b3=1, b2=1, b1=0, b0=0 → Vout ≈ 2.519 V
- Full-scale (11111) → Vout ≈ 4.688 V


Transient Simulation:

- Vout increases smoothly as binary code increments.
- Maximum observed Vout ≈ 4.88 V (close to ideal 5 V).


5-bit DAC Schematic:

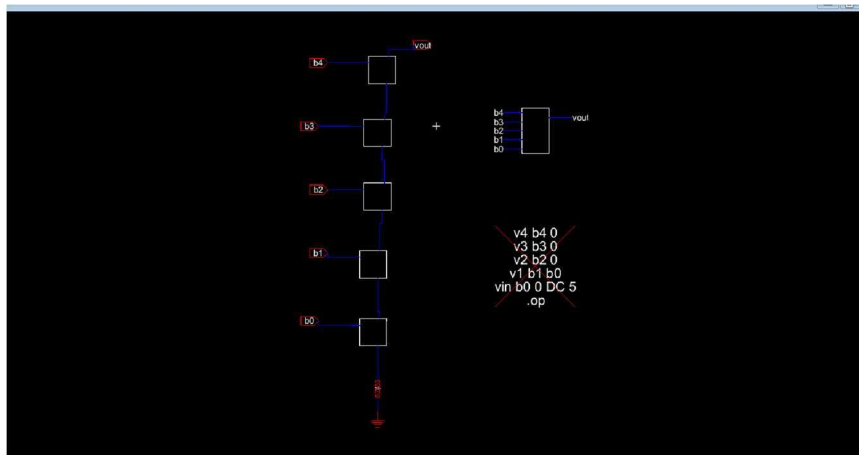


5-bit DAC Layout:

 


5-bit DAC 3D Layout:

 


LTspice Simulation - Transient Response:

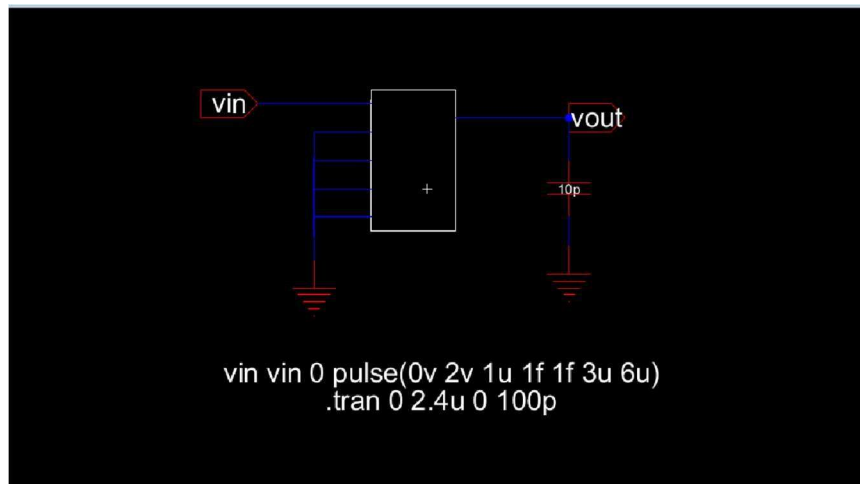


LTspice Simulation - Final Result:

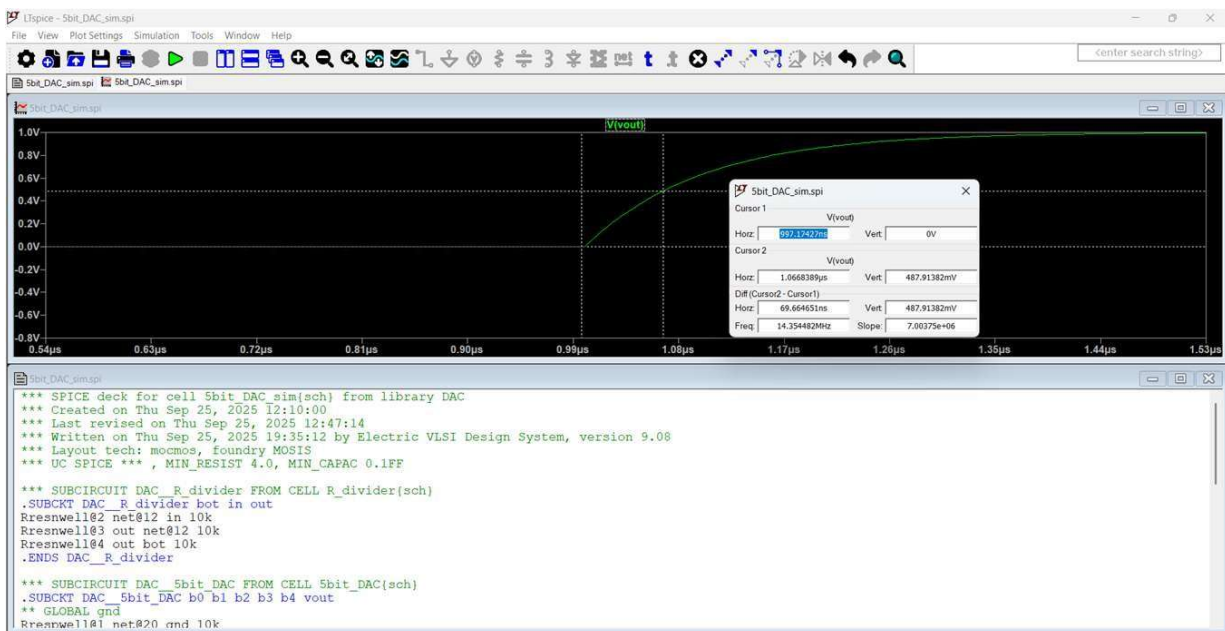

 LTspice Simulation– with 10k load connected to the DAC:



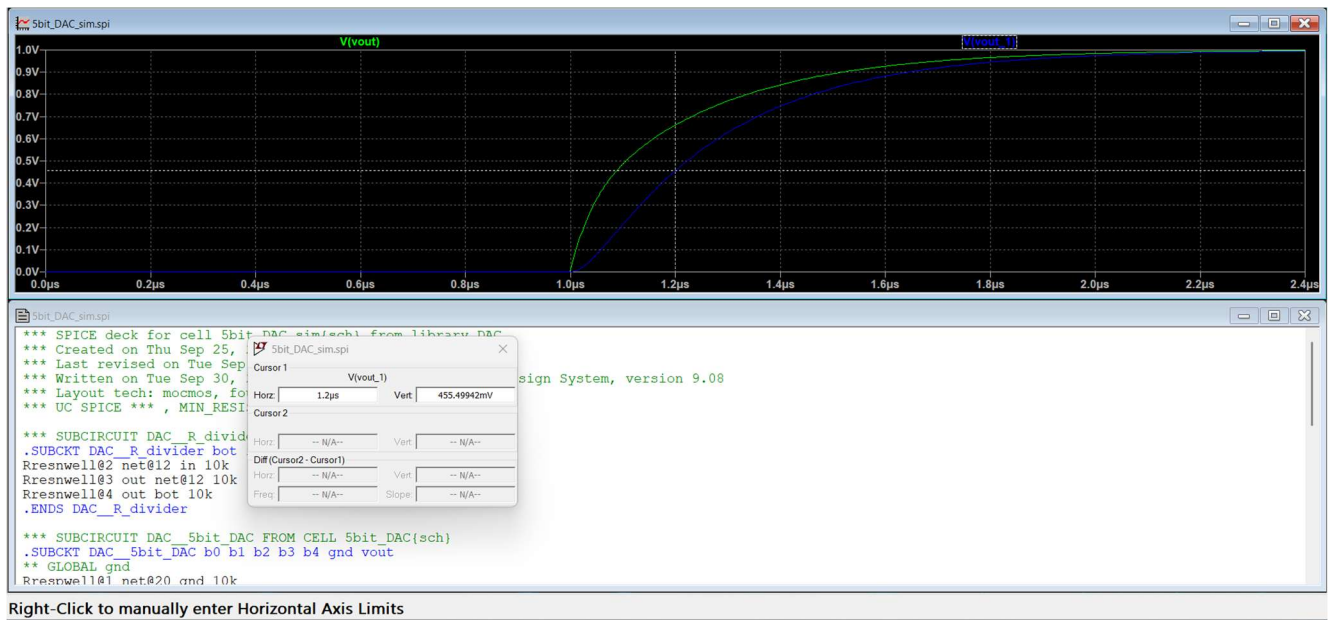

what would happen if the DAC drives 10k ohm load?

The DAC's output amplitude is cut in half.
Linearity is preserved but the scale is reduced.
The load also increases power draw from the DAC.

Determining the output resistance of the dac drives.

Replacing all digital input switches with their Thévenin equivalents
Reducing the ladder step by step. R out will be about 10K ohm

Discussion

The voltage divider results matched the expected theoretical values, validating the simulation setup. The 5-bit DAC produced correct binary-weighted outputs, confirming the accuracy of the R-2R ladder design. Small deviations ($\sim 10\text{--}20\text{ mV}$) from ideal values can be attributed to simulation tolerances, resistor matching, and rounding errors in LTspice.

The R-2R DAC is efficient since it requires only two resistor values, making layout compact and scalable. However, real-world implementation depends heavily on resistor tolerance, which affects linearity and accuracy.

Conclusion

The lab successfully demonstrated the design and simulation of both a voltage divider and a 5-bit R-2R ladder DAC. The results confirm theoretical predictions, with accurate division and binary-weighted DAC outputs. This validates the use of the R-2R structure for efficient and scalable DAC design.

References

- Lab 1: R-2R Resistor Ladder DAC

- LTspice User Manual
- Electric VLSI Documentation